Modeling Logic Gates with Delay- Part#2

by George Lungu

- In the previous section of this tutorial we concluded that in order to be able to simulate with decent precision delay in single-stage logic gates, we only need to introduce a propagation delay caused solely by rise or fall time. This makes the model of a single-stage gate fairly simple and easy to program in a single spreadsheet cell, using built-in formulas (hence making the model much faster than employing user defined functions). - This second half of the tutorial derives the final formulas and a delay based model is implemented in Excel 2003.

The simplified equivalent model:

- We use the model to the right, which (as we will see) can be written using spreadsheet built-in functions in a single cell without the need to use (very slow) user defined functions =>>>>

 In the previous series of tutorials about ideal logic gates we have already seen how to describe an inverter and a few other ideal logic gates in equations.

Let's now see how we can combine that the ideal logic gate description with a numerical low pass filter solution.

A 1-pole Low Pass Filter numerical solution:

- This topic was treated on this blog before, therefore it will be treated lightly here.

In order to numerically model
 a time dependant process we first
 need to sample its time function
 at discrete intervals dt = h

- Most of the physical processes can be described by differential equations. For easy solutions we need to find a way of expressing derivatives in an approximate but easy way. The easiest way would be to approximate the tangent to the curve in point T with the secant to the curve (there are three options available).







The first transistor - invented at Bell Labs in 1947

Three ways of approximating the tangent (first derivative) to a curve:

- To the left there are three different ways of simple approximations to the tangent using the actual value of the function in various points in time.

F

С

- Let's use the forward estimate to numerically solve the system below:



$$u_{in}(t) - u_{out}(t) = R$$

From of current intensity definition: i =

From the capacitance definition:

$$\begin{array}{l} \hline \textbf{Definition:} \quad \frac{df(t)}{dt} = \lim_{dt \to 0} \left[\frac{f(t+dt) - f(t)}{dt} \right] \\ \hline \textbf{Forward estimate:} \quad \frac{df(t)}{dt} \approx \frac{f(t+h) - f(t)}{h} \\ \hline \textbf{Backward estimate:} \quad \frac{df(t)}{dt} \approx \frac{f(t) - f(t-h)}{h} \\ \hline \textbf{Central estimate:} \quad \frac{df(t)}{dt} \approx \frac{f(t+h) - f(t-h)}{2 \cdot h} \\ \hline \textbf{Pay attention to colors} \end{array}$$

$$\left. \begin{array}{c} R \cdot i \\ \frac{dq}{dt} \\ C = \frac{dq}{du_{out}} \end{array} \right\} \implies u_{in}(t) - u_{out}(t) = R \cdot C \underbrace{\frac{du_{out}}{dt}}_{u_{in}(t) - u_{out}(t) = R \cdot C} \underbrace{\frac{u_{out}(t+h) - u_{out}(t)}{h}}_{u_{in}(t) - u_{out}(t) = R \cdot C} \underbrace{\frac{u_{out}(t+h) - u_{out}(t)}{h}}_{u_{out}(t) = R \cdot C}$$

After some minor algebraic manipulation we reach the final formula for $u_{out}(t)$:

$$u_{out}(t+h) = \frac{h}{R \cdot C} \cdot [u_{in}(t) - u_{out}(t)] + u_{out}(t)$$

The equation is valid for any moment in time. Moving it back one time step "h" (which means t = t-h) we get:

$$u_{out}(t) = \frac{h}{R \cdot C} \cdot \left[u_{in}(t-h) - u_{out}(t-h)\right] + u_{out}(t-h)$$

The final formulas for seven different logic gate models with delay:

$$\begin{split} u_{out_INV}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(u_A(t-h) > \frac{vdd}{2}, 0, vdd \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_AND}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) > \frac{vdd}{2}, u_B(t-h) > \frac{vdd}{2} \right), vdd, 0 \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NAND}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) > \frac{vdd}{2}, u_B(t-h) > \frac{vdd}{2} \right), 0, vdd \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_OR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), 0, vdd \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), 0, vdd \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), 0, vdd \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), 0, vdd \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), 0, vdd \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), vdd, 0 \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), vdd, 0 \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), vdd, 0 \right) - u_{out}(t-h) \right] + u_{out}(t-h) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), vdd, 0 \right) - u_{out}(t-h) \right] \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[if \left(u_A(t-h) < \frac{vdd}{2} \right), u_A(t-h) < \frac{vdd}{2} \right) + u_{out_NOR}(t) \right] \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[u_{out_NOR}(t) + u_{out_NOR}(t) \right] \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[u_{out_NOR}(t) \right] \\ u_{out_NOR}(t) \\ u_{out_NOR}(t) \\ u_{out_NOR}(t) &= \frac{h}{R \cdot C} \cdot \left[u_{out_NOR}(t) \right] \\ u_{out_NOR}(t) \\ u_{out_NOR}(t) \right] \\ u_{out_NOR}(t) \\ u_{out_NOR}(t) \\ u_{out_NOR$$

$$u_{out_XOR}(t) = \frac{h}{R \cdot C} \cdot \left[if \left(OR \left(AND \left(u_A(t-h) > \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) > \frac{vdd}{2} \right) \right), vdd, 0 \right) - u_{out}(t-h) \right] + u_{out}(t-h)$$

$$u_{out_XNOR}(t) = \frac{h}{R \cdot C} \cdot \left[if \left(OR \left(AND \left(u_A(t-h) > \frac{vdd}{2}, u_B(t-h) < \frac{vdd}{2} \right), AND \left(u_A(t-h) < \frac{vdd}{2}, u_B(t-h) > \frac{vdd}{2} \right) \right), vdd, 0 \right) - u_{out}(t-h) \right] + u_{out}(t-h)$$

Excel 2003 implementation:

- Copy the last file "Logic_Gates.xls" and rename the new file "Gate_Delay.xls"
- Delete the first four worksheets and leave only the last one named "Basic_4"
- Rename the remaining worksheet: "Seven_Gates_with_Delay"
- Insert a new name for cell A21: "r_c" and type a "0.5" in cell A21.
- Change the formulas in the following cells:
- Cell D37: "=time_step*(IF(B38>vdd/2,0,vdd)-D38)/r_c+D38"
- Cell E37: "=time_step*(IF(AND(B38>vdd/2,C38>vdd/2),vdd,0)-E38)/r_c+E38"
- Cell F37: "=time_step*(IF(AND(B38>vdd/2,C38>vdd/2),O,vdd)-F38)/r_c+F38"
- Cell G37: "=time_step*(IF(AND(B38<vdd/2,C38<vdd/2),O,vdd)-G38)/r_c+G38"</p>
- Cell H37: "=time_step*(IF(AND(B38<vdd/2,C38<vdd/2),vdd,0)-H38)/r_c+H38"
- Cell 137: "=time_step*(IF(OR(AND(B38>vdd/2,C38<vdd/2),AND(B38<vdd/2,C38>vdd/2)),vdd,0)-138)/r_c+138"
- Cell J37: "=time_step*(IF(OR(AND(B38>vdd/2,C38<vdd/2),AND(B38<vdd/2,C38>vdd/2)),O,vdd)-J38)/r_c+J38"
- After all these formula alterations copy range D37:J37 down to row 837 and you are ready to test the model.



<u>Running and testing the animated model:</u>

- The snapshots are taken at the following values of RC (r_c) constants : 0.2ns, 0.6ns and 2ns.

- The speed of the model is confirmed very good, namely 663 frames/minutes with the chart visible and 5168 frames/minute with the chart out of sight. This is because no user defined functions were used throughout the model.



 $RC = 0.2 \ ns$





 $RC = 0.7 \, ns$

The end

RC = 3 ns